

d)

$$I = \frac{q}{t}$$

$$q = It$$

$$= (12.5 \text{ A}) \left(15 \text{ min} \times \frac{60 \text{ s}}{1 \text{ min}} \right)$$

$$= 1.1 \times 10^4 \text{ C}$$

$$\#e^- = \frac{\text{total charge}}{\text{charge}/e^-}$$

$$= \frac{1.1 \times 10^4 \text{ C}}{1.60 \times 10^{-19} \text{ C}}$$

$$= 7.0 \times 10^{22}$$

15.

$$V = \frac{\Delta E}{q}$$

$$\Delta E = qV$$

$$= (2.4 \times 10^3 \text{ C})(120 \text{ V})$$

$$= 2.9 \times 10^5 \text{ J}$$

Lesson 3—Electric Circuits

1. In a series circuit:

$$I_T = I_1 = I_2 = I_3$$

$$I_1 = 1.7 \text{ A}$$

$$I_2 = 1.7 \text{ A}$$

$$I_3 = 1.7 \text{ A}$$

2. In a parallel circuit:

$$I_T = I_1 + I_2$$

$$I_T = 2.1 \text{ A} + 1.5 \text{ A}$$

$$= 3.6 \text{ A}$$

In a series circuit:

$$I_T = I_3$$

$$I_3 = 3.6 \text{ A}$$

3. In a series circuit:

$$V_T = V_1 + V_2$$

$$12.0 \text{ V} = 8.0 \text{ V} + V_2$$

$$V_2 = 4.0 \text{ V}$$

4. In a parallel circuit:

$$V_T = V_1 = V_2$$

$$20.0 \text{ V} = 20.0 \text{ V} = V_2$$

$$V_2 = 20.0 \text{ V}$$

5. In a series circuit:

$$V_T = V_1 + (V_2 + V_3)$$

$$45.0 \text{ V} = 11.0 \text{ V} + (V_2 + V_3)$$

$$V_2 + V_3 = 45.0 \text{ V} - 11.0 \text{ V}$$

$$= 34.0 \text{ V}$$

In a parallel circuit:

$$V_T = V_2 = V_3$$

$$34.0 \text{ V} = V_2 = V_3$$

$$V_2 = 34.0 \text{ V}$$

$$V_3 = 34.0 \text{ V}$$

6. In a series circuit:

$$R_T = R_1 + R_2$$

$$= 15.0 \Omega + 20.0 \Omega$$

$$= 35.0 \Omega$$

7. In a parallel circuit:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{6.0 \Omega} + \frac{1}{8.0 \Omega}$$

$$R_T = 3.4 \Omega$$

8. In a parallel circuit:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{3.0 \Omega} + \frac{1}{6.0 \Omega}$$

$$R_T = 2.0 \Omega$$

In a series circuit:

$$R_T = R_1 + \left(\frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$= 2.0 \Omega + 2.0 \Omega$$

$$= 4.0 \Omega$$

9.

$$R_T = R_1 + R_2 + R_3$$

$$= 9.0 \Omega + 3.0 \Omega + 12.0 \Omega$$

$$= 24.0 \Omega$$

10. In a parallel circuit:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$= \frac{1}{2.0 \Omega} + \frac{1}{4.0 \Omega} + \frac{1}{8.0 \Omega}$$

$$R_T = 1.1 \Omega$$

$$\frac{R_3}{R_2} = \frac{4.0 \, \Omega}{2.0 \, \Omega} = 2.0$$

If the resistance R_3 is 2.0 times the resistance R_2 , then the current through R_3 is 0.5 times the current through R_2 .

$$I_T = I_{R_2} + I_{R_3}$$

Let I_2 = current through R_3 .

$$2.7 \, \text{A} = 2I_2 + I_2$$

$$3I_2 = 2.7 \, \text{A}$$

$$I_2 = \frac{2.7 \, \text{A}}{3} \\ = 0.91 \, \text{A}$$

b)

$$P = I^2 R \\ = (2.7 \, \text{A})(7.3 \, \Omega) \\ = 55 \, \text{W}$$

17. a) In a series circuit:

$$R_T = R_1 + R_2 + R_3 \\ = 2.0 \, \Omega + 2.5 \, \Omega + 3.0 \, \Omega \\ = 7.5 \, \Omega \\ V = IR \\ = (8.0 \, \text{A})(7.5 \, \Omega) \\ = 6.0 \times 10^1 \, \text{V}$$

b)

$$P = I^2 R \\ = (8.0 \, \text{A})^2 (7.5 \, \Omega) \\ = 4.8 \times 10^2 \, \text{W}$$

18. a) In a parallel circuit:


$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} \\ = \frac{1}{8.0 \, \Omega} + \frac{1}{10.0 \, \Omega} \\ R_T = 4.4 \, \Omega \\ I = \frac{V}{R} \\ = \frac{25.0 \, \text{V}}{4.4 \, \Omega} \\ = 5.6 \, \text{A}$$

b)


$$P = I^2 R \\ = (5.6 \, \text{A})^2 (4.4 \, \Omega) \\ = 1.4 \times 10^2 \, \text{W}$$

Lesson 4—Magnetism


1. a)

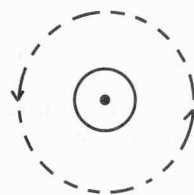


b)

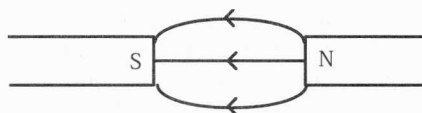


c)

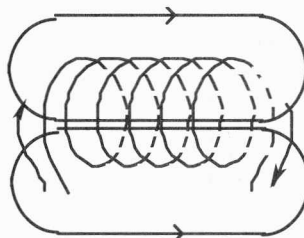


d)

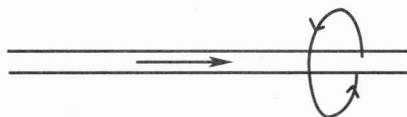

e)

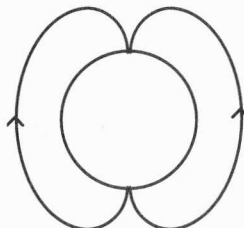

f)

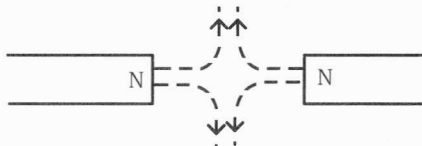

2. a) $B\alpha = \frac{I}{r}$

\therefore since r doubles, B will be $\frac{1}{2}$.

$$\text{Magnetic field at } B = \frac{1}{2}(1.5 \times 10^{-2} \, \text{T}) \\ = 7.5 \times 10^{-3} \, \text{T}$$

b) $N = \mu_0 nI$, \therefore if the current triples, the magnetic field triples.

c) $B = \mu nI$. Since the permeability (μ) increases 5 000 times, the magnetic field strength will increase 5 000 times.