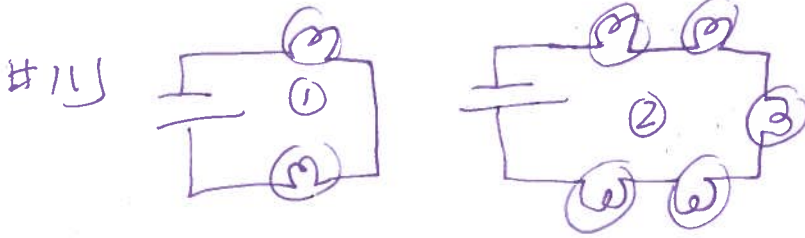


Answers to Circuit Practice Textbook Problems

1/2

11.2 #1, 11.3 Practice Problems




a) Circuit 1 would have a larger current as it has a lower total resistance (fewer bulbs connected in series)

b) Bulbs would glow brighter in circuit 1 as the power converted by each bulb is greater ($P = I^2 R$). Since the total current is greater.

11.3

Practice 1

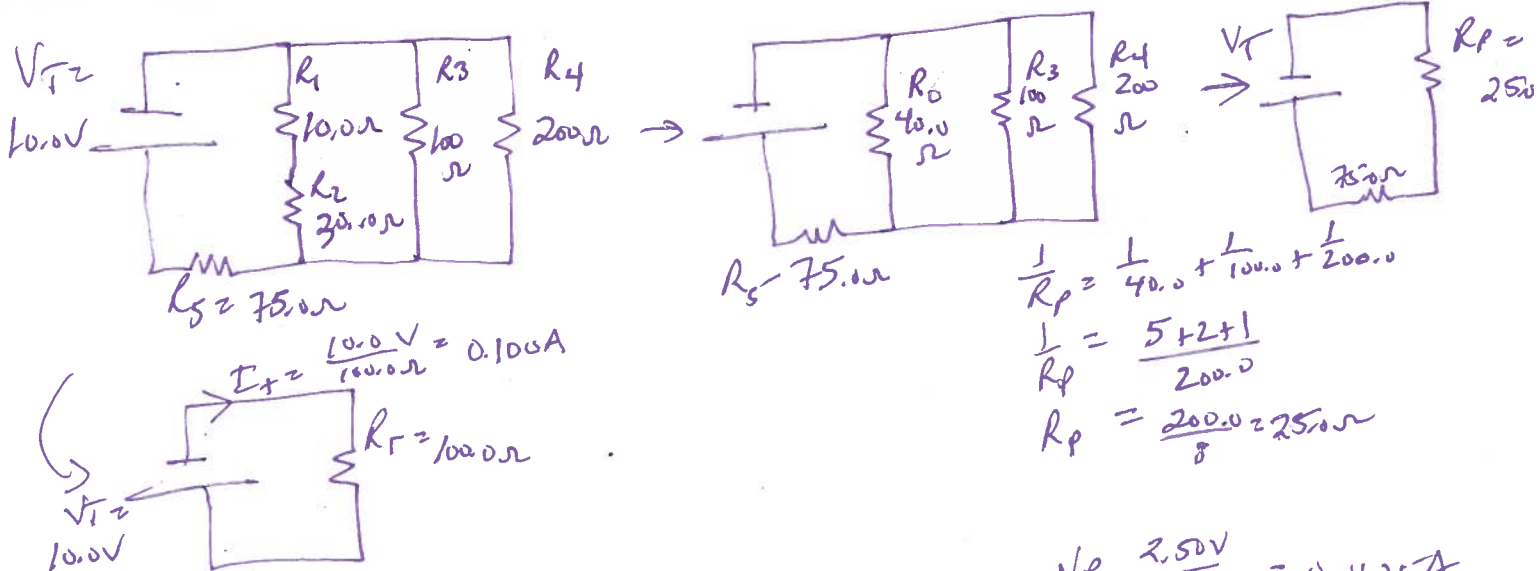

$$V_p = I_T R_p = (0.100A)(25.0\Omega) = 2.50V$$

$$V_5 = 10.0V - 2.50V = 7.50V$$

$$V_1 = I_1 R_1 = (0.0625)(10.0\Omega) = 0.625V$$

$$V_2 = I_2 R_2 = (0.0625)(30.0\Omega) = 1.875V$$

$$V_3 = V_4 = 2.50V$$

$$I_0 = \frac{V_p}{R_0} = \frac{2.50V}{40.0\Omega} = 0.0625A$$


$$I_3 = \frac{V_p}{R_3} = \frac{2.50V}{100.0\Omega} = 0.0250A$$

$$I_4 = \frac{V_p}{R_4} = \frac{2.50V}{200\Omega} = 0.0125A$$

$$I_1 = I_2 = 0.0625$$

$$I_5 = I_T = 0.100A$$

Proble 2


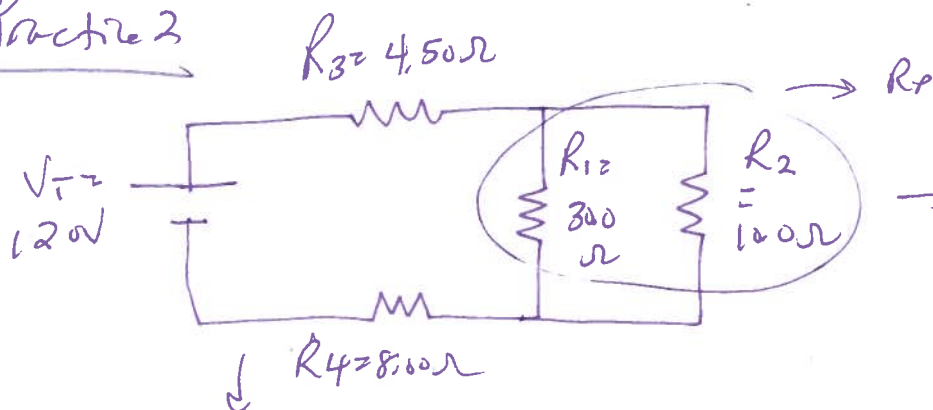


$$\frac{1}{R_p} = \frac{1}{30.0} + \frac{1}{10.0}$$

$$\frac{1}{R_p} = \frac{1}{30.0} + \frac{3}{30.0}$$

$$\frac{1}{R_p} = \frac{4}{30.0}$$

$$R_p = \frac{30.0}{4} = 7.50\Omega$$

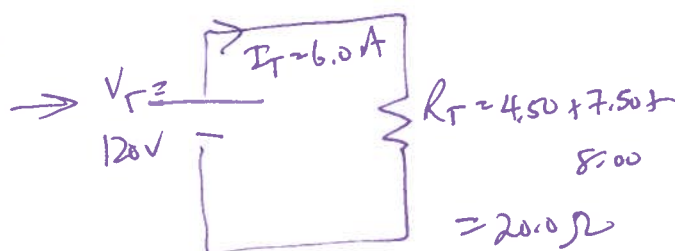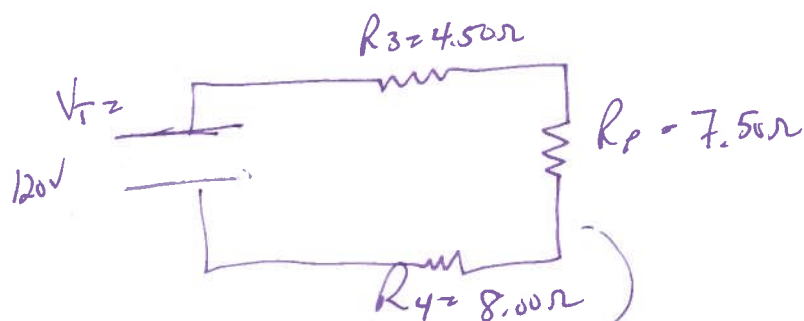

$$V_p = I_T R_p = (6.0\text{A})(7.50\Omega) = 45.0\text{V}$$

$$V_3 = I_T R_3 = (6.0\text{A})(4.50\Omega) = 27.0\text{V} \rightarrow I_3 = 6.0\text{A}$$

$$V_4 = I_T R_4 = (6.0\text{A})(8.00\Omega) = 48.0\text{V} \rightarrow I_4 = 6.0\text{A}$$

$$I_1 = \frac{V_p}{R_1} = \frac{45.0\text{V}}{(30.0\Omega)} = 1.5\text{A}$$

$$I_2 = \frac{V_p}{R_2} = \frac{45.0\text{V}}{(10.0\Omega)} = 4.5\text{A}$$