

Answer Key

Electricity Unit

Name: _____
Date: _____

Ohm's Law Calculations

$$V = IR$$

1. A heating element operates on 115 V. If it has a resistance of $12.0\ \Omega$, what current passes through the element?

$$9.58\text{ A}$$

2. A coffee pot operates on 12.0 V. If it draws 2.50 A, find its resistance.

$$4.8\ \Omega$$

3. An electric heater draws a maximum of 14.0 A. If its resistance is $15.7\ \Omega$, to what voltage should it be connected?


$$220\text{ V}$$

4. What is the potential difference does a toaster have if it has a resistance of $17.6\ \Omega$ and a current of 12.5 A passing through the toaster?


$$220\text{ V}$$

Understanding Series and Parallel Circuits

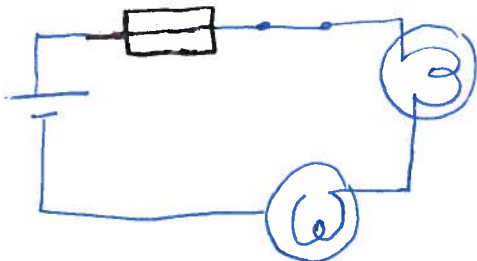
1. Draw a series circuit using symbols for a source, a fuse, a switch, 2 lamps and conducting wires.



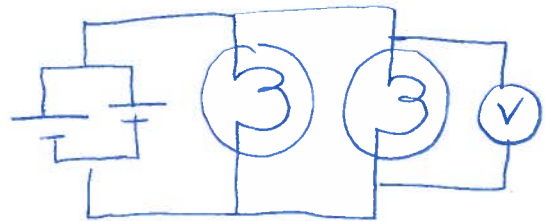
2. Draw 2 cells hooked in parallel with 2 lights and a voltmeter to measure the voltage for one of the light bulbs.



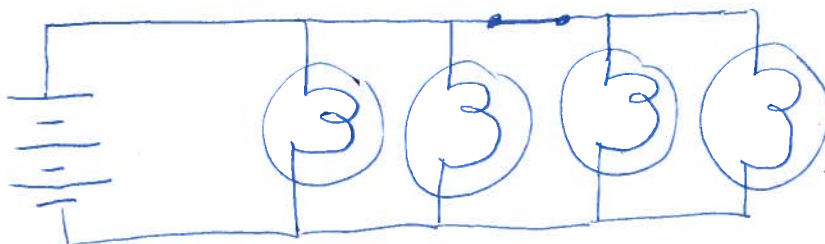3. Draw 3 cells hooked in series with 4 lights in parallel and one switch that turns off 2 of the lights.



3. Type of circuit: SERIES
Equations:

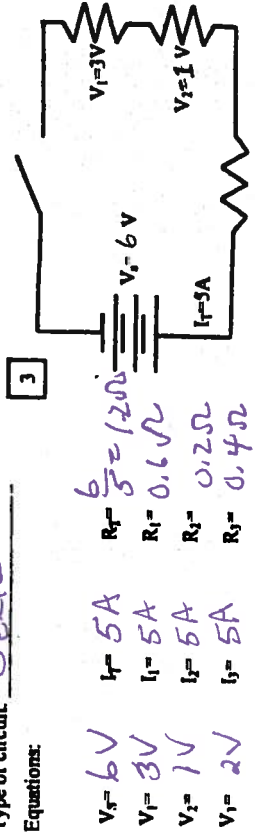


$$V_3 = V_T - (V_1 + V_2)$$

$$= 6V - 3V - 1V$$

$$= 2V$$

4. Type of circuit: PARALLEL
Equations:

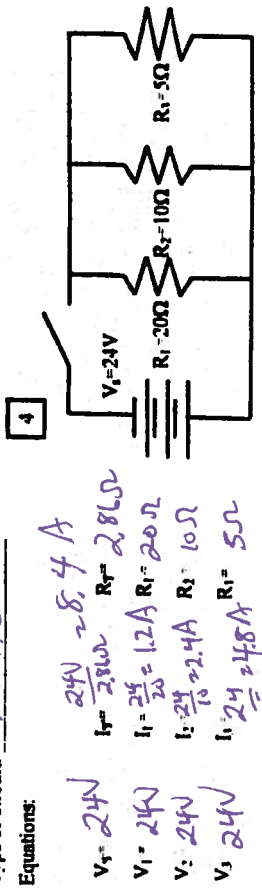


$$\frac{1}{R_T} = \frac{1}{10} + \frac{1}{10} + \frac{1}{10}$$

$$\frac{1}{R_T} = \frac{3}{10}$$

$$R_T = \frac{10}{3} = 3.33\Omega$$

Identify the type of circuit and find the missing values for each of the circuits shown below.

1. Type of circuit: SERIES
Equations:

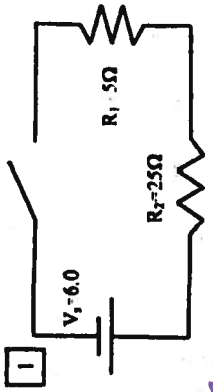

$$V_T = 6.0V$$

$$I_T = 0.20A$$

$$R_T = R_1 + R_2$$

$$= 5 + 25$$


$$= 30\Omega$$

$$V_T = 5.0V$$

$$I_T = 0.20A$$

$$R_T = 25\Omega$$

2. Type of circuit: Parallel
Equations:

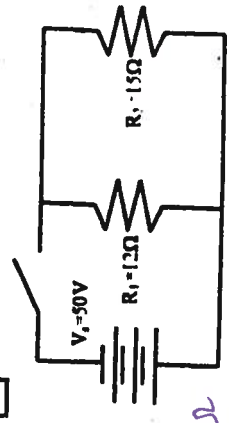

$$V_T = 30V$$

$$I_T = 6.67A$$

$$R_T = 4.17\Omega$$

$$\frac{1}{R_T} = \frac{1}{12} + \frac{1}{15}$$

$$= \frac{5 + 4}{60} = \frac{9}{60}$$

$$R_T = \frac{60}{9} = 6.67\Omega$$