

Knowledge: _____ / 20 marks

Application: _____ / 20 marks

Useful Formulas:

$$I = \frac{Q}{\Delta t} \quad V = \frac{E}{Q} \quad E = VI\Delta t \quad R_s = R_1 + R_2 + R_3 + \dots \quad \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$


$$P = IV = I^2 R = \frac{V^2}{R}$$

Part A: Multiple Choice [6 marks]

1	2	3	4	5	6
A	C	C	B	D	C

Part B: Knowledge Short Answer [14 marks]

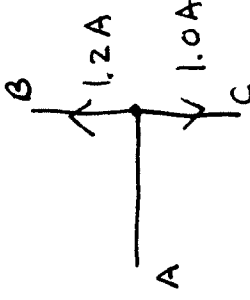
1. What is Kirchoff's Current Law and what does it tell you about the current in branch A and the junction shown below? [2]



The total current in Branch A is equal to the sum of the current in branches B + C.

$$I_A = I_B + I_C = 1.2 + 1.0 = 2.2 \text{ A}$$

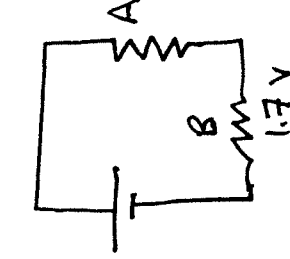
2. What is Kirchoff's Voltage Law and what does it tell you about the voltage across load A in the circuit below? [2]



The sum of the voltage drops around the circuit is equal to the total voltage gains.

$$\therefore V_T = V_A + V_B \quad \therefore V_A = 5.0 \text{ V} - 1.7 \text{ V} \\ \text{OR } V_A = V_T - V_B = 3.3 \text{ V}$$

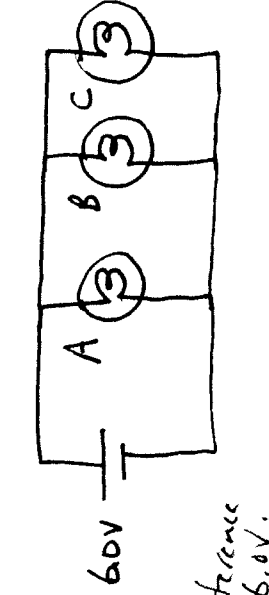3. What is/are the voltage(s) across Light Bulbs A, B and C in the circuit below? Explain your answer. [2]



The bulbs A, B and C are all in parallel with the battery.

They all see the same potential difference of 6.0V.

4. How much energy does a 1.5 V battery give 2.0 Coulombs of charge if the current is 1.5 A? [3]

$$V = 1.5 \text{ V} \quad E = V \cdot Q \quad \therefore \text{the total energy transferred is } 3.0 \text{ J.} \\ Q = 2.0 \text{ C} \quad = (1.5 \text{ V})(2.0 \text{ C}) \\ I = 1.5 \text{ A} \quad = 3.0 \text{ J} \\ E = ? \quad = 3.0 \text{ J}$$


5. A current of 540 mA flows through a flashlight bulb with a potential difference of 6.0 V across it. How much electrical energy is converted by the bulb in a time of 20.0 seconds. [5]

$$I = 0.540 \text{ A} \quad E = V I \Delta t \quad \therefore 6.5 \text{ J} \\ V = 6.0 \text{ V} \quad = (6.0 \text{ V})(0.540 \text{ A})(20.0 \text{ s}) \quad \text{electrical energy} \\ \Delta t = 20.0 \text{ s} \quad = 64.8 \text{ J.} \quad \text{is converted by} \\ E = ? \quad \sim 6.5 \text{ J} \quad \text{the bulb.}$$


Part B: Application Questions [20 marks]

1. Use Kirchhoff's Current and Voltage Laws to determine all unknown currents and voltages in the following circuits. Show your work in the space beside the diagram.

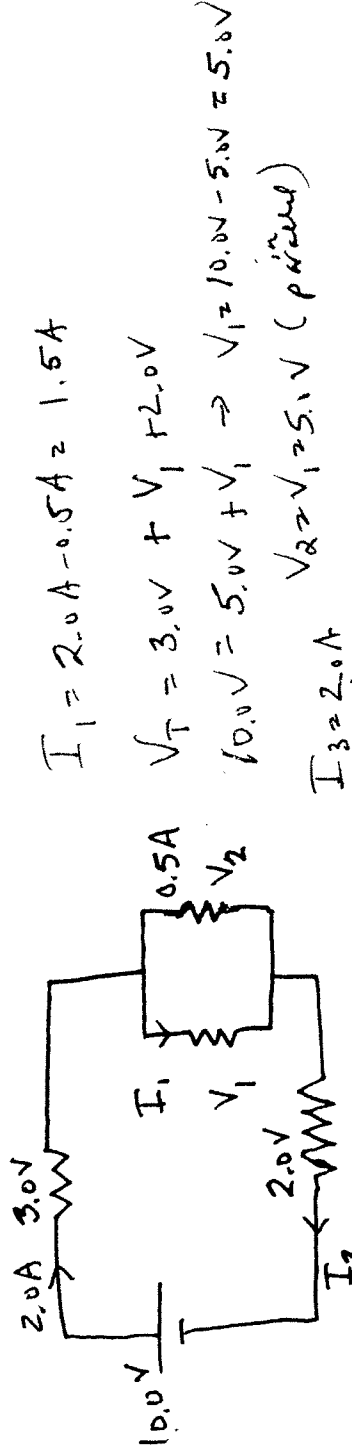
a) $I_1 = 1.5A$ $V_1 = 5.0V$ $V_2 = 5.0V$ $I_3 = 2.0A$ [4]



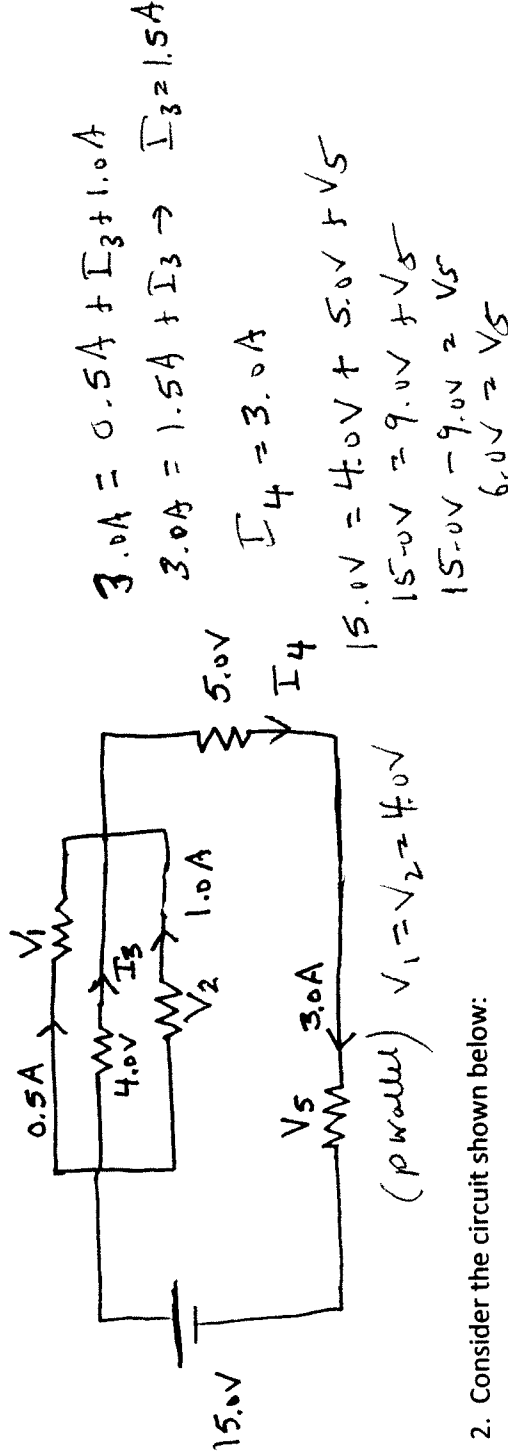b) $V_1 = 4.0V$ $V_2 = 4.0V$ $I_3 = 1.5A$ $I_4 = 3.0A$ $V_5 = 6.0V$ [5]



2. Consider the circuit shown below:

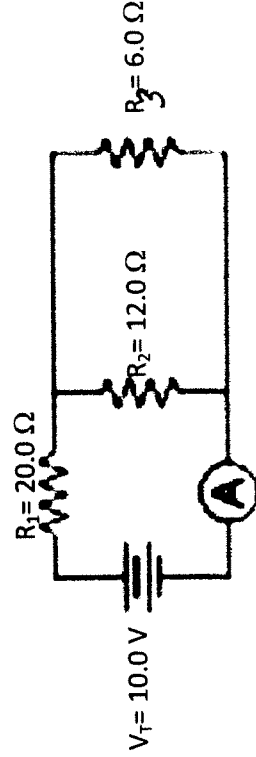

a) Solve for the total equivalent resistance in the circuit below:

Find R_p : $\frac{1}{R_p} = \frac{1}{R_2} + \frac{1}{R_3}$ Find R_T : $R_T = R_1 + R_p$
 $\frac{1}{R_p} = \frac{1}{12} + \frac{1}{6.0}$ $= 20.0\Omega + 4.0\Omega$
 $R_p = \frac{3}{12.0}$ $= 24.0\Omega$
 $R_p = 4.0\Omega$ \therefore the total equivalent resistance is 24.0Ω [2]

b) Find the total current flowing through the ammeter.

$V_T = 10.0V$ $I_T = \frac{V_T}{R_T} = \frac{10.0V}{24.0\Omega} = 0.417A$ \therefore the current is $0.417A$.
 $R_T = 24.0\Omega$
 $I_T = ?$ [2]

c) Find the voltage across resistor R_1 and the power consumed by resistor R_1 .

$I_T = 0.417A$ $V_1 = I_T R_1$ $P_1 = I_T V_1$
 $R_1 = 20.0\Omega$ $= (0.417A)(20.0\Omega)$ $= (0.417A)(8.3V)$
 $V_1 = ?$ $P_1 = ?$ $= 3.475W$
 d) Find the voltage across resistor R_2 and the power consumed by resistor R_2 . $\sim 3.5W$ [3]

$V_3 = ?$ in equivalent circuit #1:

$V_T = V_1 + V_R$ $\therefore V_2 = V_3 = 1.66V$
 $V_{R_p} = V_T - V_1 = 10.0V - 8.3V$ $P = \frac{V^2}{R} = \frac{(1.66V)^2}{12.0\Omega} = 0.23W$
 $= 1.11V$ $= 0.23W$