

For each of the circuits below, Find the following:

- The equivalent resistance of the circuit if the value of each resistor is $10\ \Omega$.
- The current produced by the battery if it has a voltage of 6.0 V .
- The current and voltage drop for each individual resistor.

