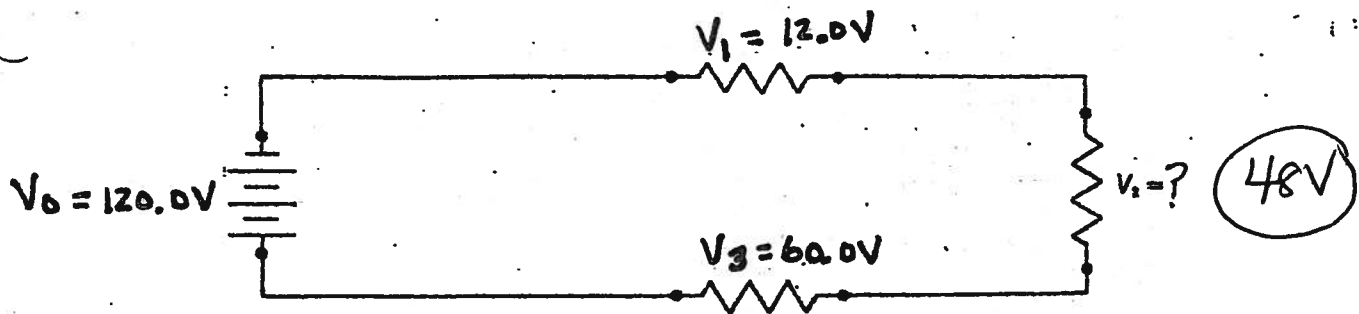



Answers

Kirchoff's Laws-Sample Problems


1. Calculate the potential difference, V_2 , in this circuit.



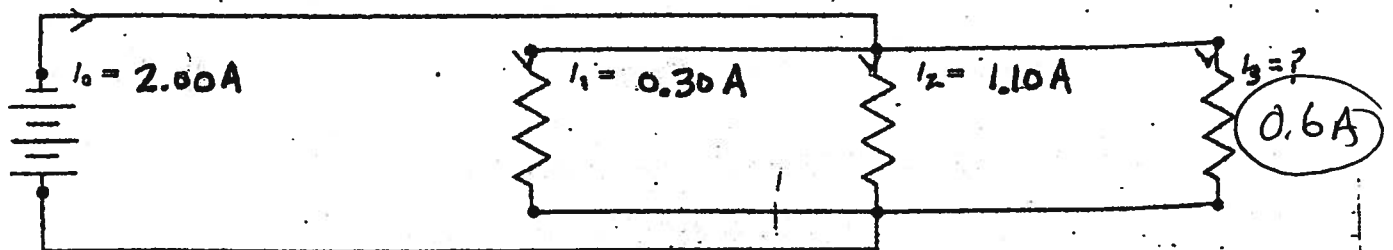
2. Calculate the electric current, I_3 , in this circuit.



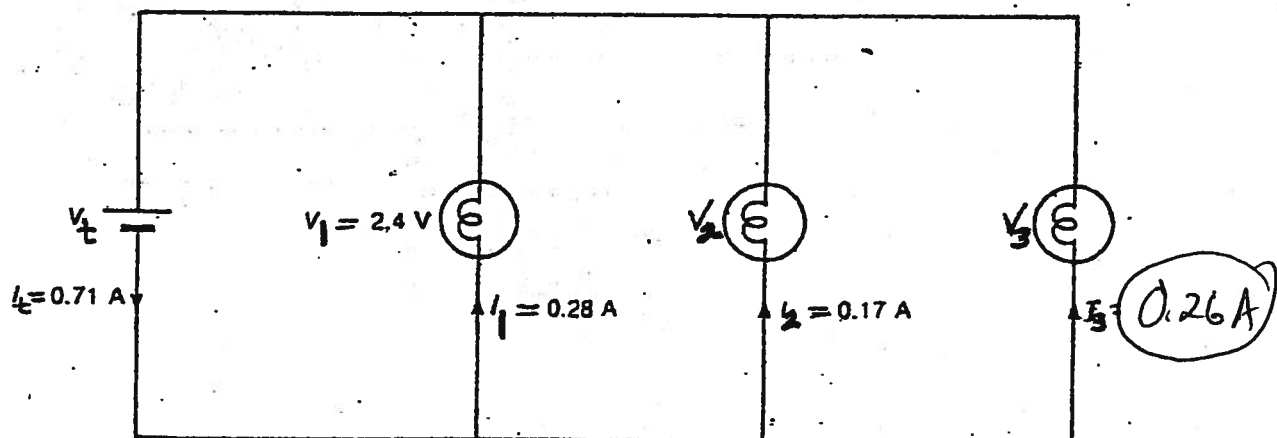3. a) Determine the unknown quantities V_1 , V_2 , V_3 and I_3 .
 b) Are the three bulbs identical?



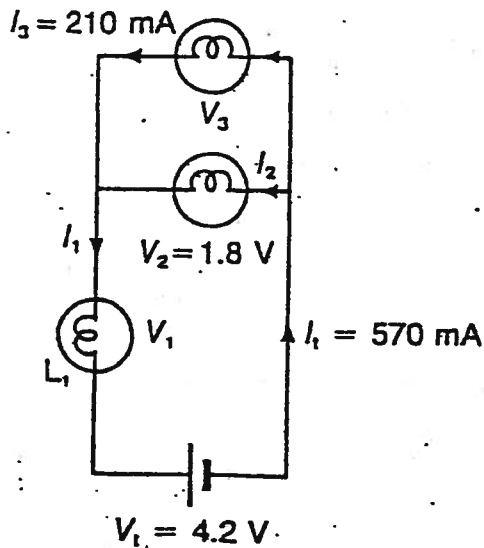4. Determine the unknown quantities, V_1 , V_3 , I_2 , I_1




$$V_3 = 1.8 \text{ V} \quad (V_2 = V_3 \text{ in parallel})$$

$$V_1 = 2.4 \text{ V} \quad (V_T = V_{2/3} + V_1)$$

$$I_2 = 360 \text{ mA} \quad (I_2 = I_t - I_3)$$

$$I_1 = 570 \text{ mA} \quad (I_1 = I_t)$$

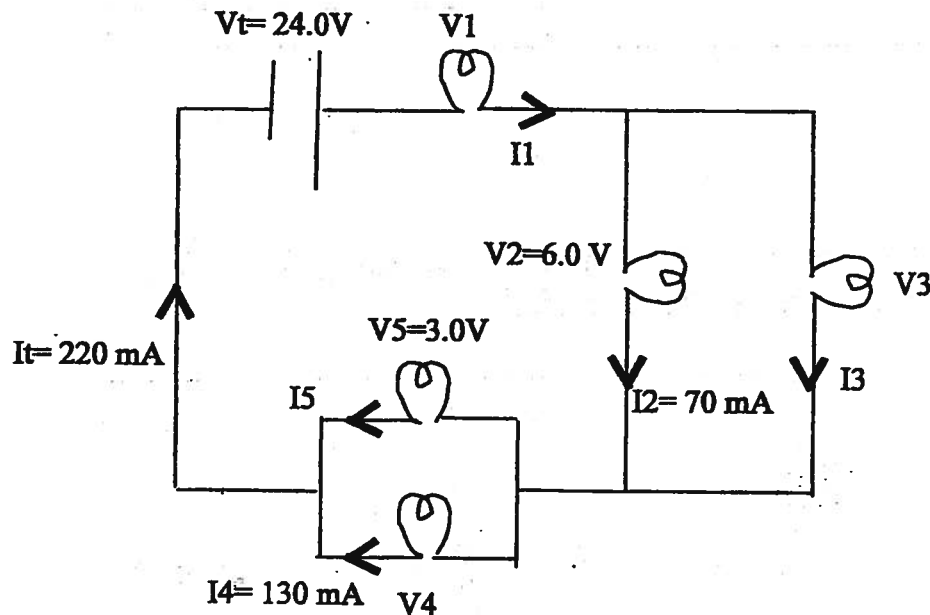5. Find V_1 , V_3 , V_4 , I_1 , I_3 and I_5 in the circuit below.



$$V_3 = V_2 = 6.0 \text{ V} \quad (\text{in parallel})$$

$$V_4 = V_5 = 3.0 \text{ V} \quad (\text{in parallel})$$

$$V_1 = 15.0 \text{ V} \quad (V_t = V_1 + V_{2/3} + V_{4/5})$$

$$I_1 = 220 \text{ mA} = I_t \quad I_3 = I_1 - I_2 \quad I_5 = I_t - I_4$$