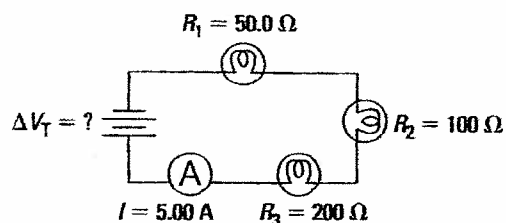


6. Explain what happens to a series circuit if one component in the circuit breaks.

A series circuit contains three resistors:  $R_1$  is  $12.0\ \Omega$ ,  $R_2$  is  $18.0\ \Omega$ , and  $R_3$  is  $45.0\ \Omega$ . A battery provides a potential difference of  $100.0\ \text{V}$ .


- What is the total resistance of the circuit?
- What current flows through the circuit?
- What is the voltage drop across each resistor?

8. Determine the potential difference across the battery and the three light bulbs shown in the following circuit diagram.





Question 8

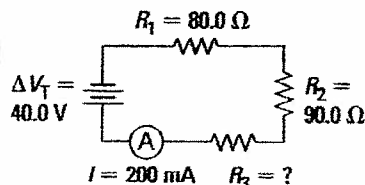9. Determine the value of the third resistor shown in the following circuit diagram.



- Two resistors are in series. Determine the resistance (in  $\text{k}\Omega$ ) provided by  $R_1$  if  $\Delta V_T = 20.0\ \text{V}$ ,  $I = 5.00\ \text{mA}$ , and  $R_2 = 1.00\ \text{k}\Omega$ . The SI prefix kilo- (k) is equal to  $10^3$ .
- All of the light bulbs shown in the circuits below are identical and have the same resistance.
  - Explain which circuit would have a larger current.
  - In which circuit would the light bulbs glow brightest? Explain your answer.

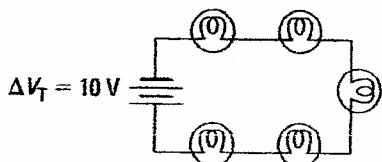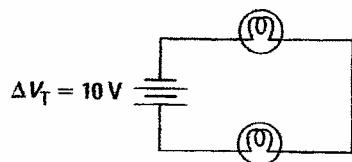

page 380, Check and Reflect 11.2

- (a)  $75.0\ \Omega$  (b)  $1.33\ \text{A}$   
(c)  $\Delta V_1 = 16.0\ \text{V}$   
 $\Delta V_2 = 24.0\ \text{V}$   
 $\Delta V_3 = 60.0\ \text{V}$
- $\Delta V_T = 1.75 \times 10^3\ \text{V}$   
 $\Delta V_1 = 250\ \text{V}$   
 $\Delta V_2 = 500\ \text{V}$   
 $\Delta V_3 = 1.00 \times 10^3\ \text{V}$
- $R_3 = 30.0\ \Omega$
- $R_1 = 3.00 \times 10^3\ \Omega$

## Practice Problems

- Determine the total resistance, total current, and the currents through each branch of the following circuit.

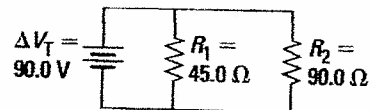


Figure 11.29

- Determine the total resistance, total current, and the currents through each branch of the following circuit.

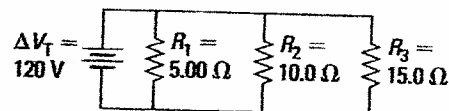


Figure 11.30

## Answers

- $R_T = 30.0\ \Omega$ ,  $I_T = 3.00\ \text{A}$   
 $I_1 = 2.00\ \text{A}$ ,  $I_2 = 1.00\ \text{A}$
- $R_T = 2.73\ \Omega$ ,  $I_T = 44.0\ \text{A}$ ,  $I_1 = 24.0\ \text{A}$   
 $I_2 = 12.0\ \text{A}$ ,  $I_3 = 8.00\ \text{A}$

## Practice Problems

- Determine the current and potential difference through each resistor in Figure 11.38.

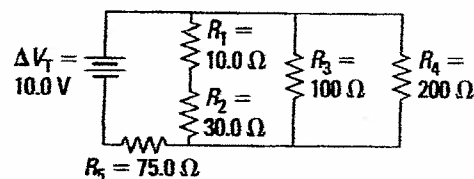


Figure 11.38

- Determine the current and potential difference through each resistor in Figure 11.39.

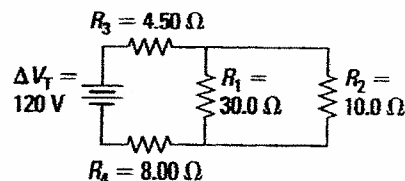


Figure 11.39

## Answers

- $I_1 = 0.0625\ \text{A}$ ,  $I_2 = 0.0625\ \text{A}$ ,  
 $I_3 = 0.0250\ \text{A}$ ,  $I_4 = 0.0125\ \text{A}$ ,  $I_5 = 0.100\ \text{A}$ ,  
 $\Delta V_1 = 0.625\ \text{V}$ ,  $\Delta V_2 = 1.88\ \text{V}$ ,  $\Delta V_3 = 2.50\ \text{V}$ ,  
 $\Delta V_4 = 2.50\ \text{V}$ , and  $\Delta V_5 = 7.50\ \text{V}$
- $I_1 = 1.50\ \text{A}$ ,  $I_2 = 4.50\ \text{A}$ ,  $I_3 = 6.00\ \text{A}$ ,  $I_4 = 6.00\ \text{A}$ ,  
 $\Delta V_1 = 45.0\ \text{V}$ ,  $\Delta V_2 = 45.0\ \text{V}$ ,  $\Delta V_3 = 27.0\ \text{V}$ ,  
and  $\Delta V_4 = 48.0\ \text{V}$

## Key Concept Review

- Copy the following table into your notebook, and fill in the cells with the appropriate equations.


Circuit Summary

Type of Circuit	Potential Difference	Resistance	Current
Series circuit			
Parallel circuit			

- What is a parallel circuit?
- Draw a circuit diagram that shows three resistors in parallel.
- What effect does increasing the number of paths in a parallel circuit have on (a) the total resistance and (b) the total current?
- If a parallel circuit develops a short circuit in one of the paths, what will happen to the current flow through the other paths?
- If a parallel circuit contains three paths, each containing resistors of exactly the same value, explain what will happen if a resistor in one of the paths burns out and does not allow current to flow.
- If two pathways in a parallel circuit have different resistances, will the current in each pathway be the same? Explain your answer.


## Connect Your Understanding

- Determine the value of  $R_2$  in the following circuit diagram.


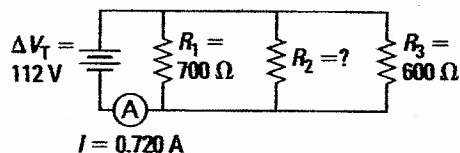


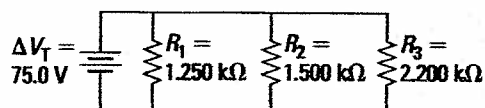Question 8

- Determine the total resistance and the current through the branches of the following circuit.




- Determine the current through the ammeter in the circuit with (a) two light bulbs in parallel and (b) after a third light bulb has been added in parallel. All light bulbs have a resistance of  $4.00 \Omega$ .

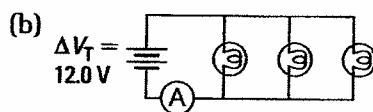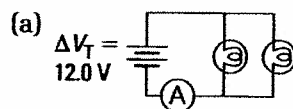


Question 10

- Determine the total current and the current through all the branches of the following parallel circuit.

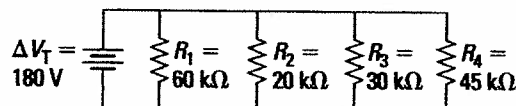

Question 11

- Determine the voltage drops and current through all the resistors in the following circuit diagram.

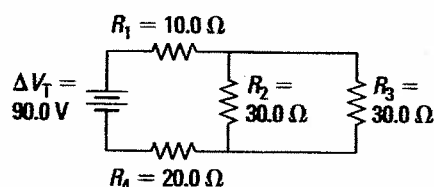

Question 12

page 389, Check and Reflect 11.3

8.  $R_2 = 300 \Omega$

9.  $R_T = 520.5 \Omega$

$I_1 = 6.00 \times 10^{-2} \text{ A}$

$I_2 = 5.00 \times 10^{-2} \text{ A}$

$I_3 = 3.41 \times 10^{-2} \text{ A}$

10. (a)  $6.00 \text{ A}$  (b)  $9.00 \text{ A}$

11.  $I_T = 0.022 \text{ A}$

$I_1 = 0.0030 \text{ A}$

$I_2 = 0.0090 \text{ A}$

$I_3 = 0.0060 \text{ A}$

$I_4 = 0.0040 \text{ A}$

12.  $\Delta V_1 = 20.0 \text{ V}$   $\Delta V_3 = 30.0 \text{ V}$

$\Delta V_2 = 30.0 \text{ V}$   $\Delta V_4 = 40.0 \text{ V}$

$I_1 = 2.00 \text{ A}$   $I_3 = 1.00 \text{ A}$

$I_2 = 1.00 \text{ A}$   $I_4 = 2.00 \text{ A}$